

Experiment 1

Name: Siddhesh Sonavane

Roll no: E42007

VHDL code:

Library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use IEEE.STD_LOGIC_unsigned.ALL;

use IEEE.STD_LOGIC_arith.ALL;

entity abc is

Port (a : in STD_LOGIC_VECTOR (3 downto 0);

b : in STD_LOGIC_VECTOR (3 downto

0); s : in STD_LOGIC_VECTOR (2 downto

0);

c : out STD_LOGIC_VECTOR (3 downto 0));

end abc;

architecture Behavioral of abc is

begin

process (a,b,s)

begin

case s is

when "000" => c <= a + b;

when "001" => c <= a - b;

when "010" => c <= a and b;

when "011" => c <= a or b;

when "100" => c <= a nand b;

when "101" => c <= a nor b;

when "110" => c <= not a;

when "111" => c <= a;

when others => null;

end case;

end process;

end Behavioral;

Testbench:

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
ENTITY xyz IS
END xyz;
ARCHITECTURE behavior OF xyz IS
  COMPONENT abc
  PORT(
    a : IN  std_logic_vector(3 downto 0);
    b : IN  std_logic_vector(3 downto 0); s : IN  std_logic_vector(2 downto 0);
    c : OUT std_logic_vector(3 downto 0));
  END COMPONENT;
--Inputs
  signal a : std_logic_vector(3 downto 0) := (others => '0');
  signal b : std_logic_vector(3 downto 0) := (others => '0');
  signal s : std_logic_vector(2 downto 0) := (others => '0');
--Outputs
  signal c : std_logic_vector(3 downto 0);
BEGIN
  uut: abc PORT MAP (
    a => a,
    b => b,
    s => s,
    c => c );
  stim_proc: process
  begin
    -- hold reset state for 100 ns.
    wait for 100 ns;
    a<="1010";
    b<="1001";
    s<="000";
    wait for 100 ns;

    a<="1010";
    b<="1001";
    s<="000";
    wait for 100 ns;
    a<="1010";
    b<="1001";
    s<="001";
    wait for 100 ns;
    a<="1010";
    b<="1001";
    s<="010";
    wait for 100 ns;
    a<="1010";
    b<="1001";
    s<="101";
    wait for 100 ns;
    a<="1010";
    b<="1001";
    s<="100";
    wait for 100 ns;
    a<="1010";
    b<="1001";
    s<="101";
    wait for 100 ns;
    a<="1010";
    b<="1001";
    s<="110";
    wait for 100 ns;
    a<="1010";
    b<="1001";
    s<="111";
    wait for 100 ns;
    --- wait for <clock>_period*10;
    -- insert stimulus here
  wait;
end process;
END;
```

ISE Project Navigator (P.15xf) - D:\sakshiHadder\bitalu\bitalu.xise - [abc (RTL2)]

File Edit View Project Source Process Tools Window Layout Help

Design

View: Implementation Simulation

Hierarchy

- bitalu
 - xc3s400-5pq208
 - abc - Behavioral (abc.vhd)

No Processes Running

Processes: abc - Behavioral

- Design Summary/Reports
- Design Utilities
- User Constraints
- Synthesize - XST
 - View RTL Schematic
 - View Technology Schematic
 - Check Syntax
 - Generate Post-Synthesis Simu...
- Implement Design
- Generate Programming File
- Configure Target Device

abc.vhd Design Summary (Synthesized) xyz.vhd abc.ngr:1 abc (RTL2)

Design Objects of Top Level Block

Instances: abc

Pins

Signals

Name Value

Activate Windows

Go to Settings to activate Windows.

[544,488]

Type here to search

25°C 10:12 19-07-2024

ISim (P.15xf) - [Default.wcfg]

File Edit View Simulation Window Layout Help

Name Value

a[3:0]	1010
b[3:0]	1001
s[2:0]	000
c[3:0]	0011

0 ns 200 ns 400 ns 600 ns 800 ns

215.172 ns

X1: 215.172 ns

Default.wcfg

Search Results

Activate Windows

Go to Settings to activate Windows.

Compilation Log Breakpoints Find in Files Results Search Results

Sim Time: 1,000,000 ps

Type here to search

10:18 19-07-2024

UCF:

net a(3) loc=p96;
net a(2) loc=p97;
net a(1) loc=p100;
net a(0) loc=p101;
net b(3) loc=p90;
net b(2) loc=p93;
net b(1) loc=p94;
net b(0) loc=p95;
net s(2) loc=p85;
net s(1) loc=p86;
net s(0) loc=p87;
net c(3) loc=p167;
net c(2) loc=p166;
net c(1) loc=p165;
net c(0) loc=p162;

RTL simulation:

The screenshot displays the ISE Project Navigator interface. The main window shows the RTL schematic for the behavioral model 'abc'. The schematic includes several logic components: an AND gate (and2), an OR gate (or2), an inverter (inv), a 4-to-1 multiplexer (MUX:1), an adder (ADDSUB:1), and a 4-to-1 multiplexer (MUX:1). The signals are connected to the pins of these components. The left pane shows the project hierarchy with 'abc - Behavioral (abc.vhd)' selected. The bottom pane shows the 'Design Objects of Top Level Block' table, which lists the instances of the components used in the design.

Instances	Pins	Signals
abc	abc	abc

Properties: (No Selection)

Errors Warnings View by Category

Zoom out such that objects become smaller

[-324,-28]

=====

* Final Report *

=====

Final Results

RTL Top Level Output File Name : abc.ngc

Top Level Output File Name : abc

Output Format : NGC

Optimization Goal : Speed

Keep Hierarchy : No

Design Statistics

IOs : 15

Cell Usage :

BELS : 34

LUT2 : 5

LUT3 : 10

LUT4 : 6

MUXF5 : 9

MUXF6 : 4

IO Buffers : 15

IBUF : 11

OBUF : 4

=====

Device utilization summary:

Selected Device : 3s400pq208-5

Number of Slices: 11 out of 3584 0%

Number of 4 input LUTs: 21 out of 7168 0%

Number of IOs: 15

Number of bonded IOBs: 15 out of 141 10% Partition Resource Summary:

No Partitions were found in this design.

Experiment No: 2

Name: Siddhesh Sonavane
Roll No.: E42007

VHDL CODE

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
ENTITY shiftreg IS
END shiftreg;
ARCHITECTURE behavior OF shiftreg IS
  COMPONENT unishiftreg
  PORT(
    si : IN std_logic; clk
    : IN std_logic; so :
    OUT std_logic;
    pin : IN std_logic_vector(3 downto 0);
    po : OUT std_logic_vector(3 downto 0);
    sel : IN std_logic_vector(1 downto 0)
  );
  END COMPONENT;
  --Inputs
  signal si : std_logic := '0';
  signal clk : std_logic := '0';
  signal pin : std_logic_vector(3 downto 0) := (others => '0');
  signal sel : std_logic_vector(1 downto 0) := (others => '0');
  --Outputs
  signal so : std_logic;
  signal po : std_logic_vector(3 downto 0);
  constant clk_period : time := 10 ns;
BEGIN
  uut: unishiftreg PORT MAP (
    si => si,
    clk => clk,
    so => so,
    pin => pin,
    po => po,
    sel => sel
  );
  clk_process : process
  begin
    clk <= '0';
    w
    a
    i
    t
    f
    o
    r
    c
    l
    k
    _
    p
    e
    r
    i
    o
    d
    /
    2
    ;
    c
    l
    k
    <
```

```
=  
,  
1  
,  
  
stim_proc: process  
begin  
    wait for 100 ns;  
    wait for clk_period*10;  
end process;  
  
END;
```

TestBench:

LIBRARY ieee;

USE ieee.std_logic_1164.ALL;

ENTITY tb IS

END tb;

ARCHITECTURE behavior OF tb IS

COMPONENT unishiftreg

PORT(

si : IN std_logic; clk

: IN std_logic; so :

OUT std_logic;

pin : IN std_logic_vector(3 downto 0);

po : OUT std_logic_vector(3 downto 0);

sel : IN std_logic_vector(1 downto 0)

);

END COMPONENT;

--Inputs

signal si : std_logic := '0';

signal clk : std_logic := '0';

signal pin : std_logic_vector(3 downto 0) := (others => '0');

signal sel : std_logic_vector(1 downto 0) := (others => '0');

--Outputs

signal so : std_logic;

signal po : std_logic_vector(3 downto 0);

constant clk_period : time := 10 ns;

BEGIN

uut: unishiftreg PORT MAP (

si => si,

clk => clk,

so => so,


```

    pin => pin,

    po => po,

    sel => sel

);

clk_process :process

begin

    clk <= '0';

    wait for clk_period/2;

    clk <= '1';

    wait for clk_period/2;

end process;

stim_proc: process

begin

    sel <= "00";

    si <= '1';

    wait for 100 ns;

    sel <= "01";

    si <= '1';

    wait for 100 ns;

    sel <= "10";

    pin <= "1010";



    wait for 100 ns;

    wait;

end process;

END;
```

Entity:

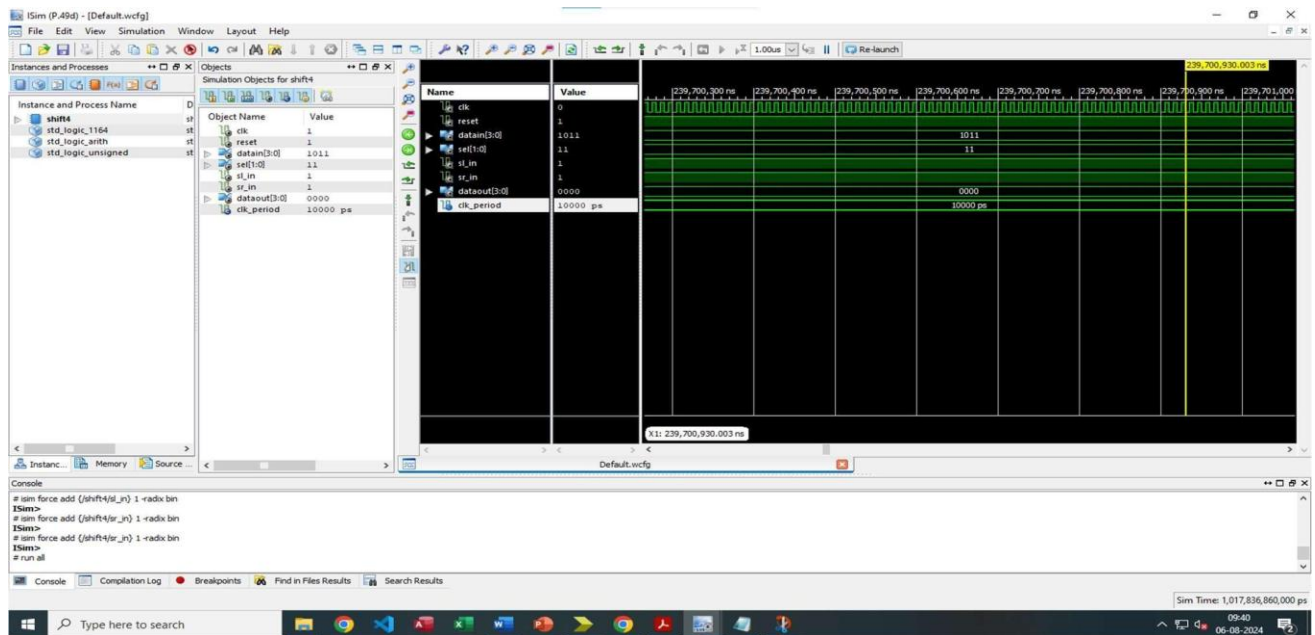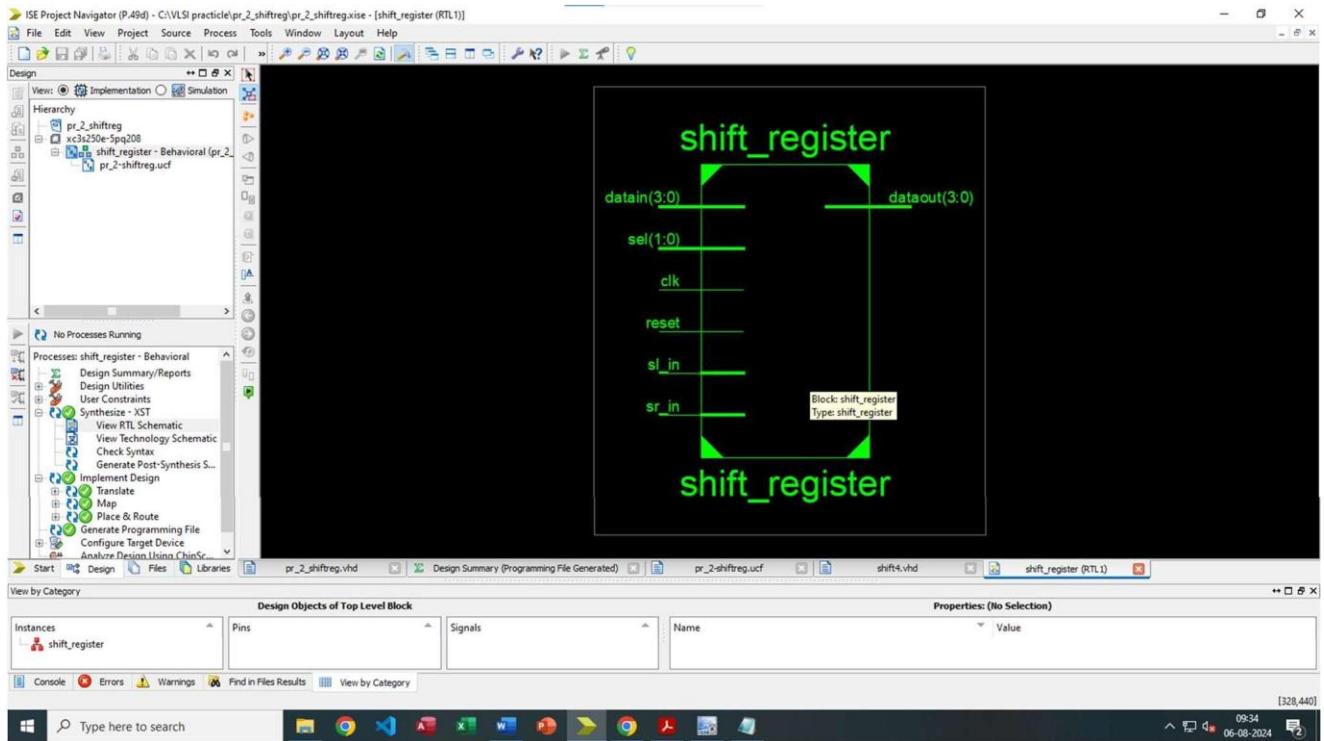

UCF File:

NET "clk" LOC = P132; NET

"reset" LOC = P204; NET

"sl_in" LOC = P179; NET

"sr_in" LOC = P180; NET

"sel<0>" LOC = P165; NET

"sel<1>" LOC = P167;

NET "datain<0>" LOC = P192;

NET "datain<1>" LOC = P193;

NET "datain<2>" LOC = P189;


NET "datain<3>" LOC = P190;

NET "dataout<0>" LOC = P205;

NET "dataout<1>" LOC = P206;

NET "dataout<2>" LOC = P203;

NET "dataout<3>" LOC = P200;

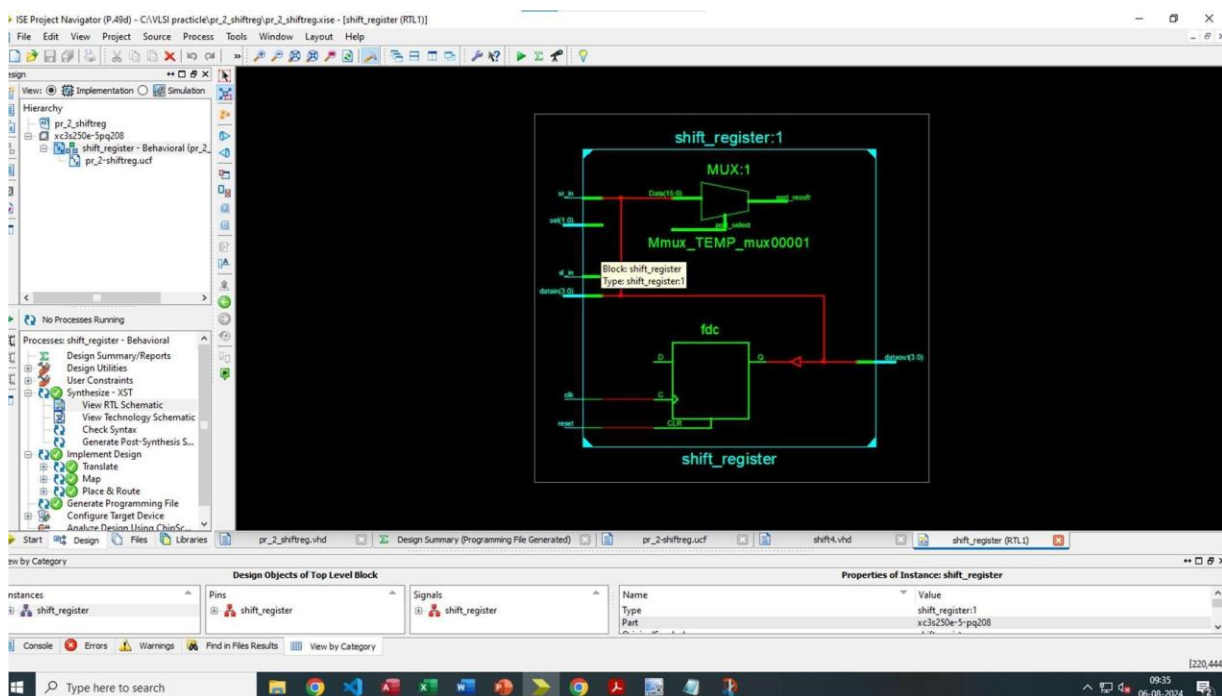

=====

* Final Report *

=====

Final Results

RTL Top Level Output File Name : unishiftreg.ngr

Top Level Output File Name : unishiftreg

Output Format : NGC

Optimization Goal : Speed

Keep Hierarchy : No

Design Statistics

IOs 13

Cell Usage :

BELS 6

LUT2 2

LUT3 4

FlipFlops/Latches 9

FD 4

FDE 5

Clock Buffers 1

BUFGP 1

IO Buffers 8

IBUF 3

OBUF 5

=====

Device utilization summary:

Selected Device : 3s400pq208-5

Number of Slices: 5 out of 3584 0%

Number of Slice Flip Flops: 9 out of 7168 0%

Number of 4 input LUTs: 6 out of 7168 0%

Number of IOs: 13

Number of bonded IOBs: 9 out of 141 6%

Number of GCLKs: 1 out of 8 12%

Partition Resource Summary:

No Partitions were found in this design.

Experiment No: 3

Name: Siddhesh Sonavane

Roll No: E42007

Testbench:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_unsigned.ALL;
entity modncount is
    Port ( clk : in STD_LOGIC;
          clr : in STD_LOGIC;
          q : inout STD_LOGIC_VECTOR (2 downto 0));
end modncount;

architecture Behavioral of modncount is
    signal count: std_logic_vector(2 downto 0);
begin
    process(clk)
    begin
        if (clr='1') then count <= "000";

    elsif (rising_edge (clk)) then
        if (count="100")
            then count <= "000";

        else
            count<=count+ 1;
        end if;
    end if;
    end process;
    q<=count;
end Behavioral;
```



Testbench:

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
ENTITY hhh IS
END hhh;

ARCHITECTURE behavior OF hhh IS
    COMPONENT modncount
    PORT(
        clk : IN std_logic;
        clr : IN std_logic;
        q : INOUT std_logic_vector(2 downto 0)
    );
    END COMPONENT;


    --Inputs
    signal clk : std_logic := '0';
    signal clr : std_logic := '0';
    signal q : std_logic_vector(2 downto 0);
BEGIN
    uut: modncount PORT MAP (
        clk => clk,
        clr => clr,
        q => q
    );
    clk_process : process
    begin
        clk <= '0';
        wait for 10 ns;
        clk <= '1';
        wait for 10 ns;
    end process;
    stim_proc: process
    begin
        clr<='1';
        wait for 20 ns;
        clr<='0';
        wait for 20 ns;
        wait;
    end process;



END;
```

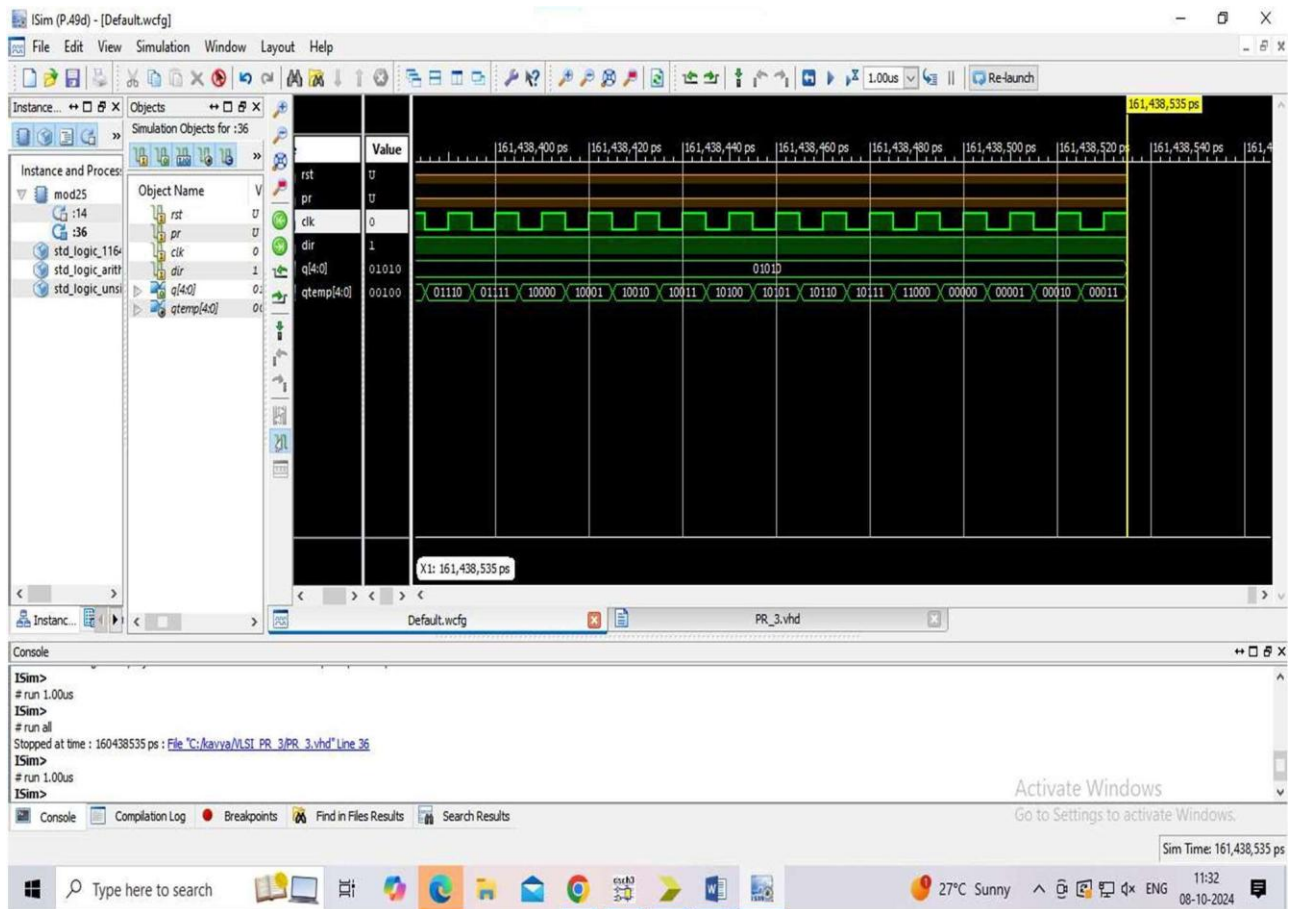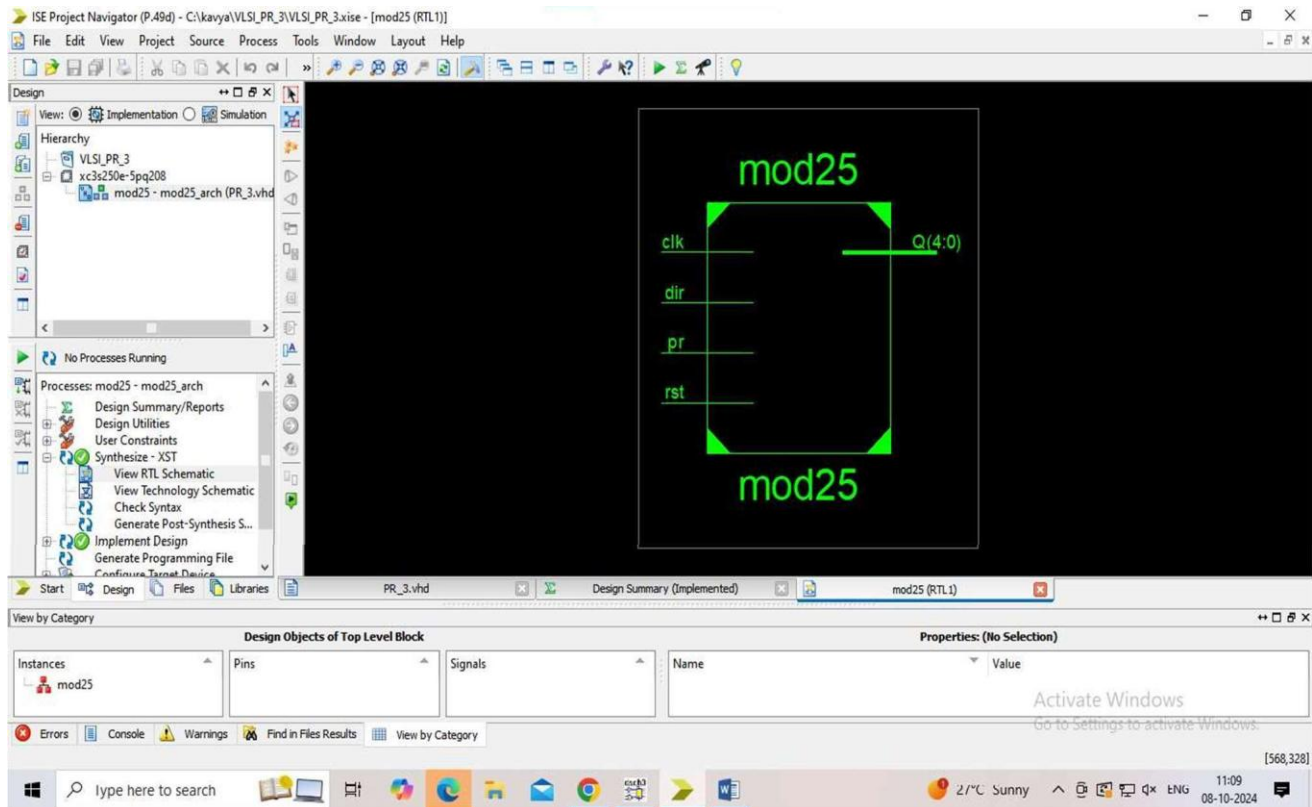

UCF

```
Net clk loc="p182";  
Net clr loc="p102";  
Net q(2) loc="p165";  
Net q(2) loc="p166";  
Net q(2) loc="p167";
```

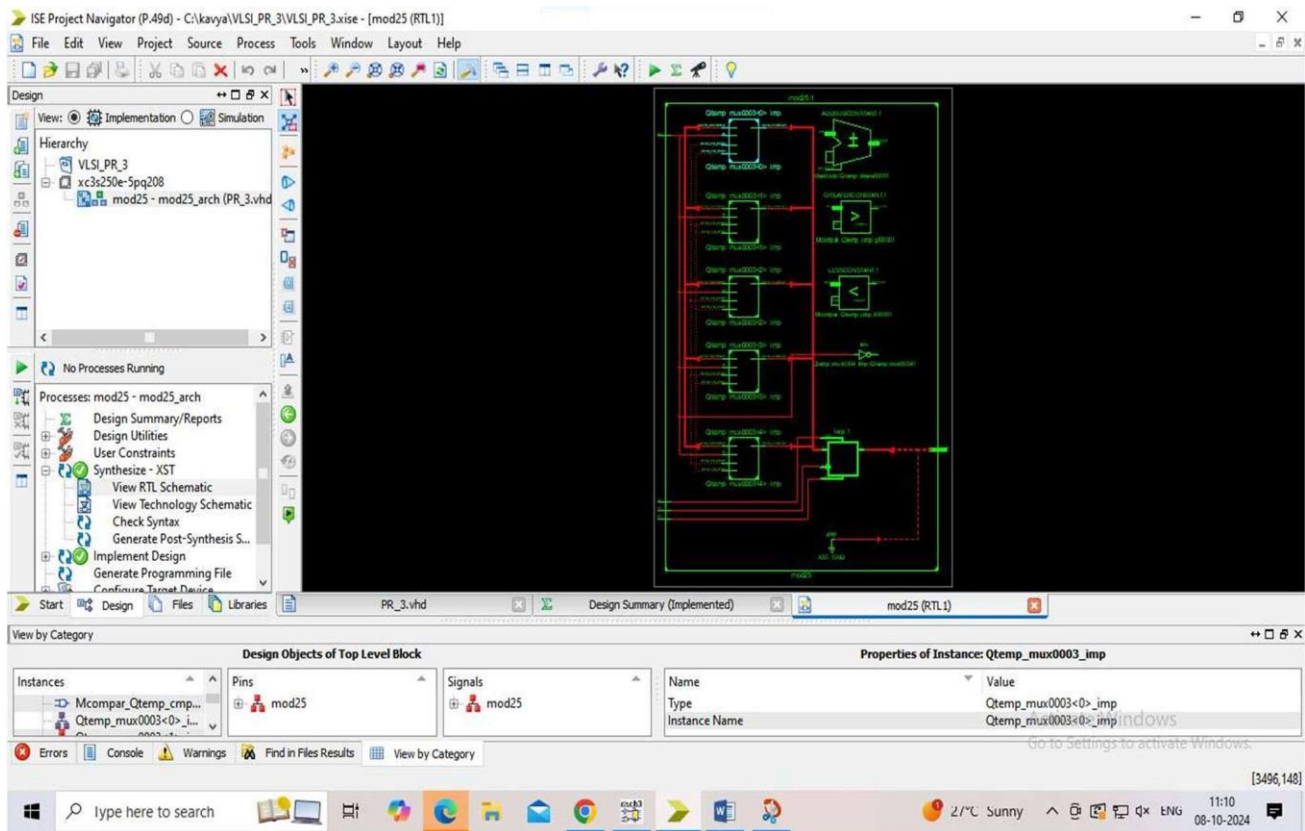

 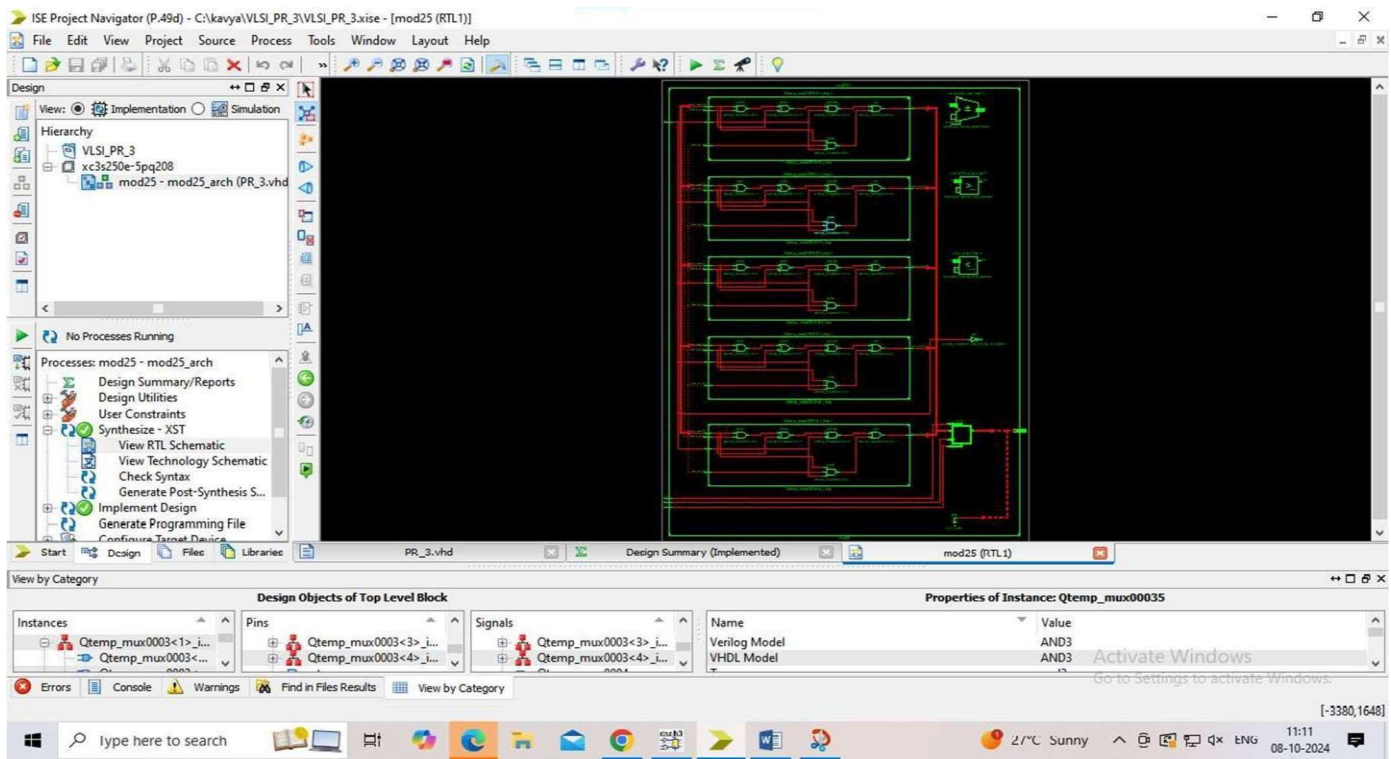

Practical 10

Name: Siddhesh Sonavane

Roll no: E42007

HALDADDER

libraryIEEE;

use IEEE.STD_LOGIC_1164.ALL;

entityHALFADDERis

Port (A : in STD_LOGIC;

B : in STD_LOGIC;

SUM : out STD_LOGIC;

CARRY : out STD_LOGIC);

endHALFADDER;


architectureBehavioralofHALFADDERis begin

SUM<=A XOR B;

CARRY<=AANDB;


endBehavioral;

HALFADDER

 

HALFADDER

HALFADDER:1

 

```

FULLADDER

libraryIEEE;



use IEEE.STD_LOGIC_1164.ALL;

entityFULLADDERis
    Port ( A : in  STD_LOGIC;
           B : in  STD_LOGIC;
           CIN : in  STD_LOGIC;
           SUM : out  STD_LOGIC;
           COUT : out  STD_LOGIC);
endFULLADDER;

architectureBehavioralofFULLADDERis begin
    component HALFADDER
    port(A:in  STD_LOGIC;
         B : in  STD_LOGIC;
         SUM : out  STD_LOGIC;
         CARRY:out  STD_LOGIC);
    endcomponent;
    signalS1,C1,C2:STD_LOGIC;
    begin
        ha1:HALFADDER port map (A,B,S1,C1);
        ha2:HALFADDERportmap(S1,CIN,SUM,C2);
        COUT<=C1 OR C2;
    end
end

```

```
endBehavioral;
```

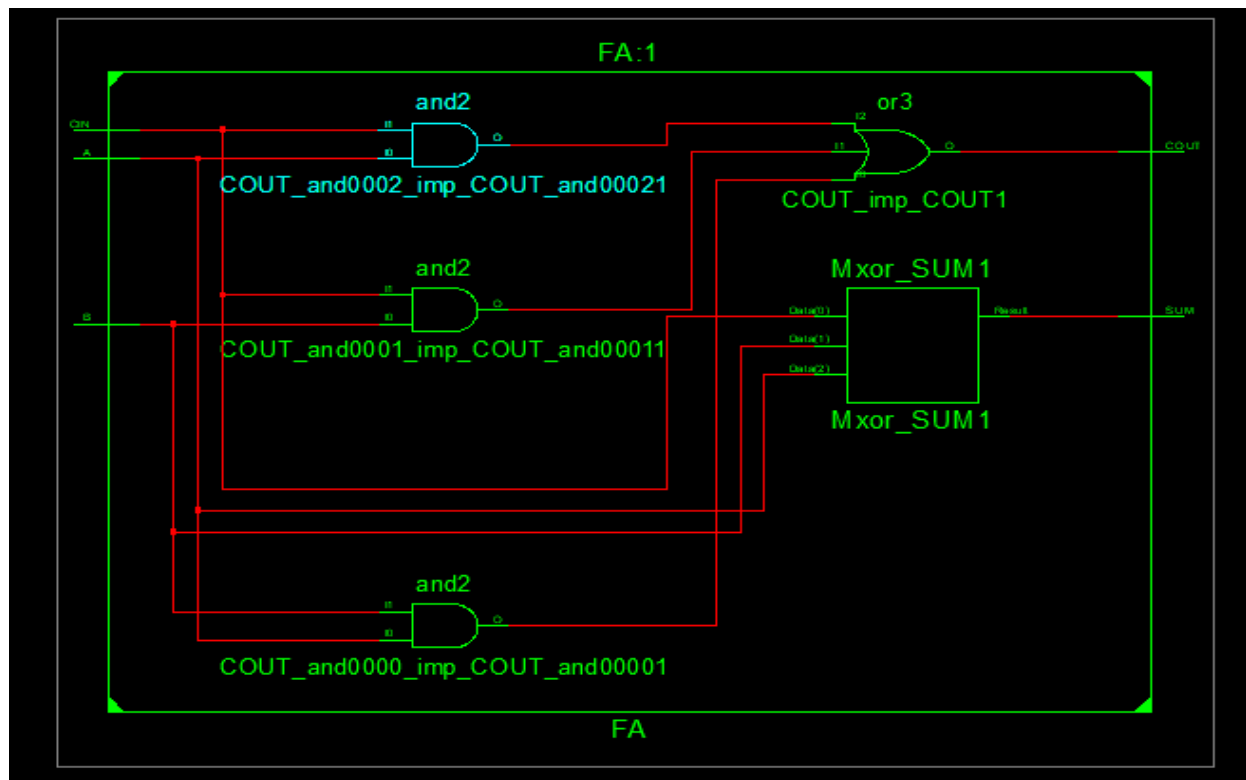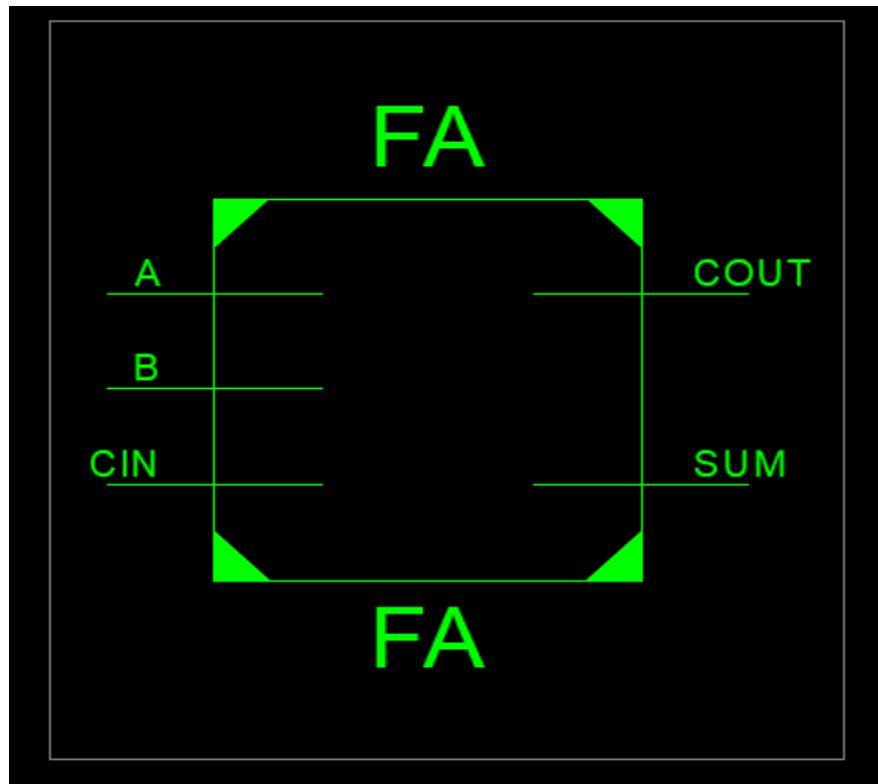

TESTBENCH

LIBRARYieee;
USEieee.std_logic_1164.ALL;

ENTITYFAAIS

END FAA;

ARCHITECTUREbehaviorOFFAAIS

--ComponentDeclarationfortheUnitUnderTest(UUT) COMPONENT

FA

PORT(

A: IN std_logic;

B : IN std_logic;

CIN : IN std_logic;

SUM : OUT std_logic;

COUT : OUT std_logic

);

ENDCOMPONENT;

--Inputs

signal A : std_logic := '0';

signal B : std_logic := '0';

signalCIN:std_logic:='0';

```

        --Outputs
        signal SUM : std_logic;
        signalCOUT:std_logic;
BEGIN
        --InstantiatetheUnitUnderTest(UUT) uut:
        FA PORT MAP (
                A=>A,
                B=>B,
                CIN => CIN,
                SUM=>SUM,
                COUT=>COUT);
        --Stimulusprocess
        stim_proc: process
        begin
                --holdresetstatefor100ns.
        A<='0';B<='0';CIN<='0';
        waitfor100ns;
        A<='0';B<='0';CIN<='1';
        waitfor100ns;
        A<='0';B<='1';CIN<='0';
        waitfor100ns;
        A<='0';B<='1';CIN<='1';
        waitfor100ns;
        A<='1';B<='0';CIN<='0';

```

```

waitfor100ns;
A<='1';B<='0';CIN<='1';
waitfor100ns;
A<='1';B<='1';CIN<='0';
waitfor100ns;
A<='1';B<='1';CIN<='1';
waitfor100ns; wait;
endprocess;

```

